February 19<sup>th</sup> 2025 Alp Efe Kılıçarslan, 22402390 EEE 102-2

## LAB-02: Introduction to VHDL

## **Purpose:**

The goal of this assignment was to debug and test a buggy project file for a BASYS3 FGPA using VHDL and Vivado. A combinational logic circuit, which is a time-independent circuit who is memoryless and whose output is determined only by it's inputs, was given as the project. With these parameters, the experimenters could get a basic introduction to VHDL and FGPA's, allowing them to understand design and implementation for future projects.

## **Design Specifications:**

The given files included one top module, two submodules and one constraint file. The constraint files assigned each switch to a specific LED on the BASYS3 in accordance to the FGPA's manual. The top module (top\_module) was the main project while that controlled the entire system. Using the constraint file and the top module, the code was made functionable. The first submodule (sub\_module1) handled what gate handled what input. The gates in this file were changed using the instructions given in the lab assignment. The second submodule (sub\_module2\_the\_beast) handled port and logic assignment for each switch and LED.

Certain variables in the code determined what each module worked with. In the first submodule, eight values were assigned to i\_input\_byte and o\_output\_byte each and were defined as logic vectors so that the logic gates were able to do the required function. The specified architecture used three 2-variable logic gates for the operation of the module.

The second module declared eight logic values for i\_switch\_inputs and o\_output\_vector in its port. These were used later on to get the input data from the BASYS3 and output the desired output LED on the same board. The declared variables were processed and later on used in the top module for the final output.

The top module included eight logic vectors for i\_SW and o\_LED in its port. i\_SW was used as the input switch parameter and o\_LED was used as the output LED's state determiner. Using the submodules' included data, these parameters were turned into usable signals and finalized the program.

# Methodology:

Four questions that were asked in the laboratory assignment were researched before any interaction with the included files. These questions and their informed answers are as follows:

- How does one specify the inputs and outputs of a module in VHDL?
- The inputs and outputs of a module are specified within the entity declaration using the port section. The port section lists all the ports along with their names, directions (in, out, or inout), and data types such as std\_logic for the given task. For example, in an entity declaration, inputs can be defined like i\_SW: in std\_logic; and o\_LED: out std\_logic;. This defines the interface for the module, and the actual functionality of the module is described in the architecture section, where the interaction between the inputs and outputs is implemented.
- How does one use a module inside another code/module? What does PORT MAP do?
- To use one module inside another, it must be instantiated within the architecture of the parent module. The PORT MAP statement is used to connect the ports of the instantiated module to the corresponding signals or variables in the parent module. This ensures that the internal signals of the instantiated module are properly linked to the external signals of the parent module, facilitating the flow of data between them. The PORT MAP statement is important for defining how inputs and outputs are routed and ensures correct interaction between the modules.
- What is a constraint file? How does it relate your code to the pins on your FPGA?
- A constraint file is used to map the logical signals in a design to specific physical pins on an FPGA. It provides the necessary information for the synthesis and implementation tools to connect the design's ports (such as inputs, outputs, and clock signals) to the corresponding FPGA pins. This file typically includes pin assignments, I/O standards, timing constraints, and other configuration details that specify how the FPGA should interact with external hardware. By using a constraint file, the logical design described in the code is tied to the physical FPGA device, ensuring proper communication with external components.
- What is the purpose of writing a testbench?
- The purpose of writing a testbench is to simulate and verify the functionality of a design before implementing it on hardware. A testbench provides a controlled environment where input signals can be applied to the design, and its outputs can be monitored and compared to expected results. Writing a testbench helps in debugging, validating the logic, and improving the overall reliability of the design.

After these questions were answered, the given tasks were done as follows:

Task-1) The first submodule file was edited according to the experimenters last ID digit. The changes made to the submodule was saved.

Task-2) The synthesis of the program was run to get the errors. After this, every file was analyzed and debugged according to the related errors and warnings. When the bugs were gotten rid of, the synthesis was run again to check if the program worked without any errors.

Task-3) The BASYS3 FGPA was connected to the computer running the code with a USB cable. A bitstream was generated for the FGPA to run on. The computer connected to the FGPA through Vivado's auto connect option. After the connection was established, the "Program Device" function was ran. After the board fully realized the written program, different states were created by using the switches on the FGPA and photographed.

Task-4) A testbench which cycled different signals sequentially was coded with the help of the laboratory's teaching assistants. The signal that was generated by the testbench was run through the top module in a simulation whose runtime was edited to accommodate the full generated signal. The testbench utilized a loop, which helped the formatting of the simulation.

Task-5) Using Vivado's built in function, the RTL schematic was formed by clicking the schematic button under RTL Analysis. Likewise, the same process was repeated under Synthesis and Implementation in order to get the synthesized and implemented design respectively. The relation between all three schematics were noted under Results on the report.

Task-6) All pieces of edited code were noted and written on the Results section of the report.

#### **Results:**

Task-1) The gates that were required to be changed were determined by the experimenter's ID's last digit. Since the digit in question was zero, an AND gate, an OR gate and an XOR gate was added to the submodule file respectively (Figure 1.1) and the changes were saved.

```
Project Summary
                   sub module1.vhd
                                    × sub module2.vhd
                                                       × top module.vhd *
                                                                                                    ? [
C:/VivadoProjects/labwork2/project_1/sub_module1.vhd
Q
                        T X //
 5
         Port (
 6
             i_input_byte : in STD LOGIC VECTOR (7 downto 0);
 7
             o_output_byte : out STD LOGIC VECTOR (7 downto 0)
 8
         );
 9 end sub module1;
10
11 architecture Structural sub1 of sub module1 is
12
    begin
13
14
        o output byte(0)
                                   <= i input byte(0) and i input byte(1); --Change these three opera</pre>
        o output_byte(1)
15
                                   <= i input byte(2) or i input byte(3);
16
         o output byte(2)
                                  <= i input byte(4) xor i input byte(5);
17
        o_output_byte(5 downto 3) <= "010";
18 !
         o_output_byte(7 downto 6) <= (others => '0');
```

Figure 1.1: Edited gates in sub module1.vhd

Task-2) Four errors were gotten after the synthesis was run and observed under the Messages tab in Vivado (Figure 2.1). Using the information from this data, the following changes were made:

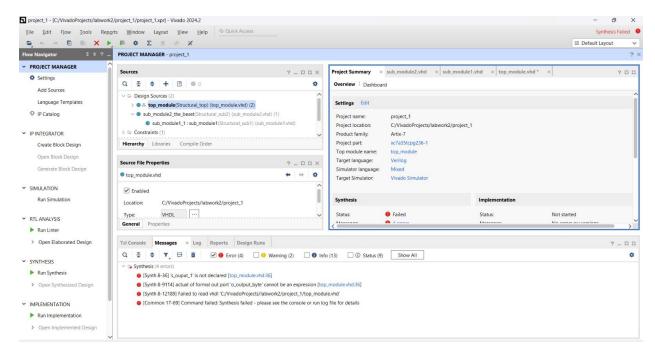


Figure 2.1: Received errors after synthesis run

1) A syntax error was located on top\_module was located and fixed by changing "s\_ouput\_1" to "s\_output\_1" (Figure 2.2),

```
× sub_module2.vhd
Project Summary
                × sub_module1.vhd
                                                      × top_module.vhd *
                                                                                                  ? 0 0
C:/VivadoProjects/labwork2/project_1/top_module.vhd
Q
                        ■ × // ■ ♀
                                                                                                      O
22
             port (
                 i_switch_inputs : in STD_LOGIC_VECTOR (7 downto 0);
23
24
                 o_output_vector : out STD LOGIC VECTOR (7 downto 0)
25
             ):
26 🖨
         end component sub module2;
27
28
         signal s output 1, s output 2 : STD LOGIC VECTOR(7 downto 0) := (others => '0');
                                     : unsigned(7 downto 0)
29
         signal s output 3
                                                               := (others => '0');
30
31
    begin
32
33 ⊖
         sub_module1_2 : sub_module1
34
             port map (
35
                i_input_byte => i_SW,
36
                 o_output_byte => s_output_1
37 🖨
38 ;
```

Figure 2.2: Line 36 of top\_module.vhd after the syntax error was removed

2) The wrong order for the port map was corrected by editing the 40<sup>th</sup> line in the top module file (Figure 2.3),

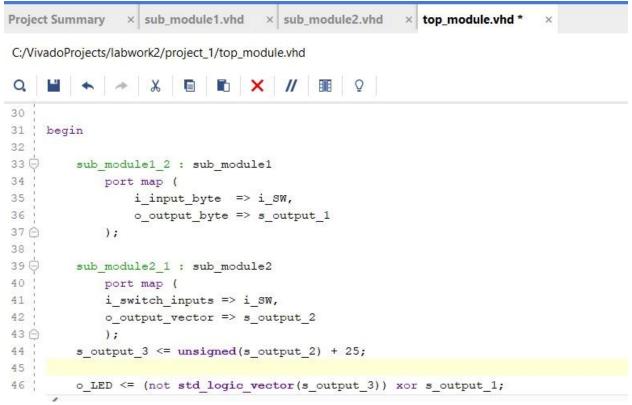


Figure 2.3: Lines 39-43 after the ordering of the program was corrected

3) Every instance of "sub\_module2" was changed to "sub\_module2\_the\_beast" due to the fact that the Sources tab in Vivado referred to the file as such (Figure 2.4),

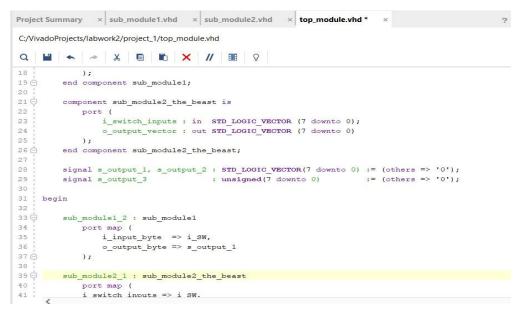


Figure 2.4: top module.vhd after editing the file to add "sub module2 the beast"

4) In the Sources tab in Vivado, the top\_module was right clicked and set as top by clicking the related button in order to get the right simulation waveform for future steps (Figure 2.5).

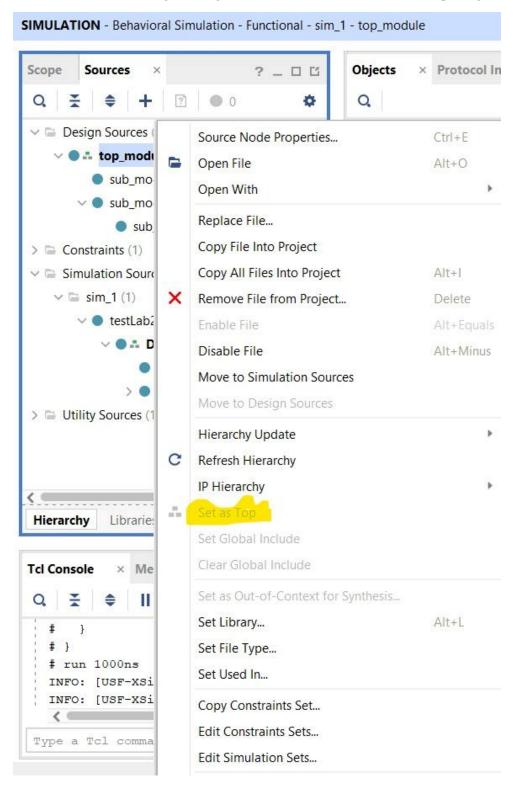


Figure 2.5: Set as Top button for top\_module.vhd highlighted after clicking

After these changes were made, no errors were observed in the Message tab of Vivado. Due to this reason, each file in the program was individually analyzed. After this analysis, two errors were observed in the constraints file. The LED layout had these errors in it. To fix these errors, the following steps were taken:

- 5) The package pin for line 24 and 38 (V14 and U16) were swapped to fit the BASYS3 manual (Figure 2.6),
- 6) A missing curly bracket in line 33 was filled in (Figure 2.6).

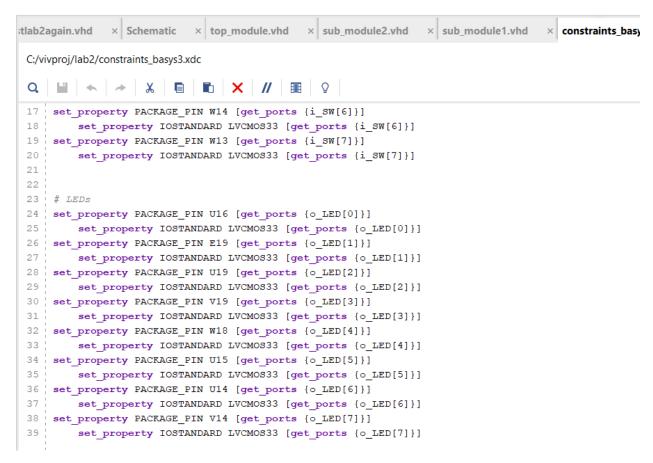


Figure 2.6: connstraints basys3.xdc after the errors were debugged

In total, six errors were debugged and the design was in a completely working state.

Task-3) After the required hardware implementations were taken -Generate Bitstream, Connect Device, Open Target, Program Device-, certain LEDs lit up on the FPGA board (Figure 3.1). On top of the default state, five more different input and output states were implemented on the BASYS3 board and observed (Figure 3.2-3.6). The observed values matched the expected results from the implemented gates.

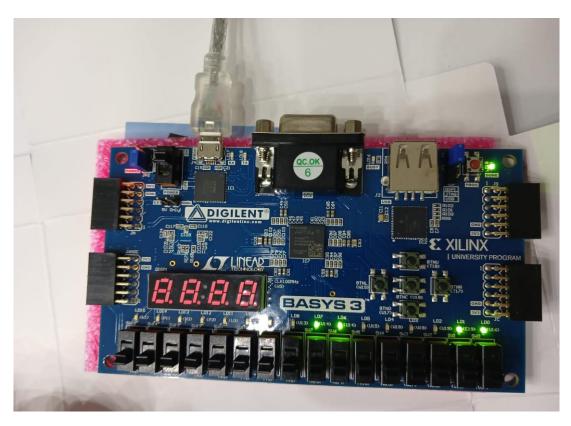


Figure 3.1: Default state of the BASYS3

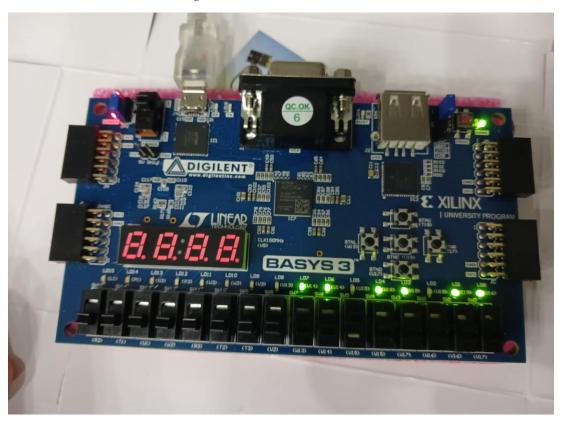


Figure 3.2: State of the BASYS3 when SW5 is on

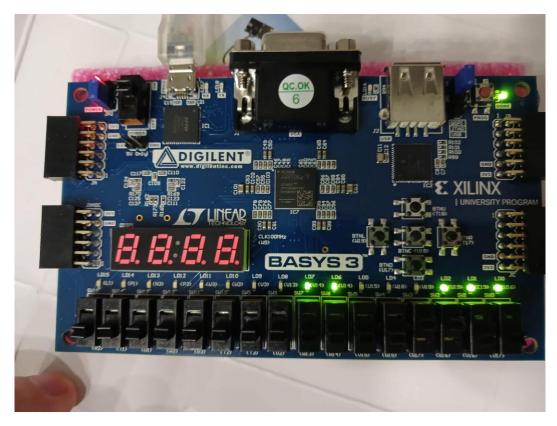


Figure 3.3: State of the BASYS3 when SW2 and SW3 are on

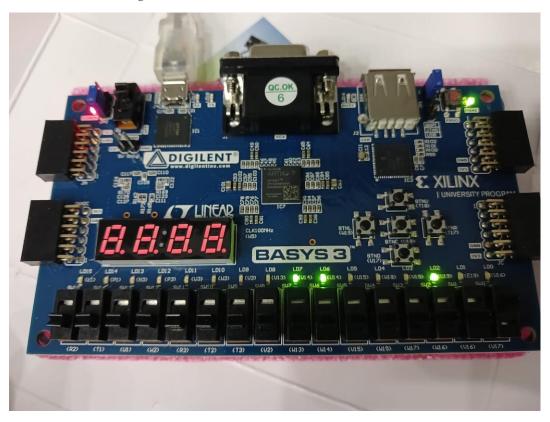


Figure 3.4: State of the BASYS3 when SW0 is on

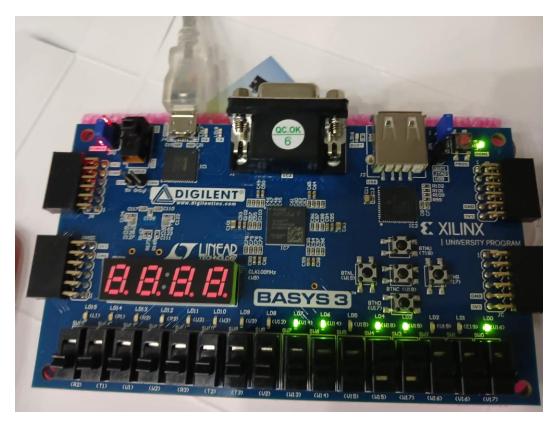


Figure 3.5: State of the BASYS3 when SW3 and SW4 are on

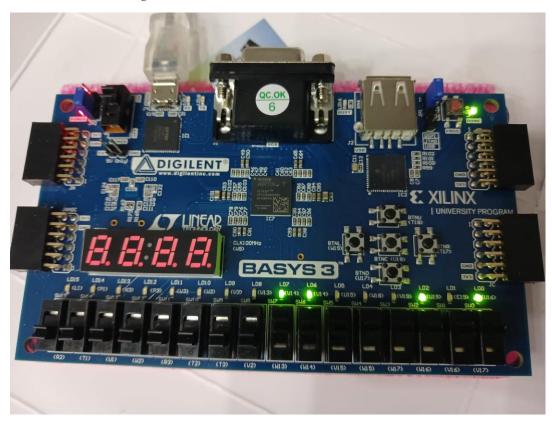


Figure 3.6: State of the BASYS3 when switches between SW0 and SW7 are on  $\,$ 

Task-4) The programmed testbench iterated through every integer between zero and two hundred and fifty-five. These products were turned into a waveform in binary in order to create a systematic waveform input that could be ran through the modules to get an environment that could be parsed freely to check the ideal outputs of the related inputs. A simulation was ran using the Run Simulation function of Vivado. Since the correct module was set to top to be simulated, no errors were ran into when the simulation was ran. A waveform configuration was observed and matched with the related input in the switch configurations that were gathered in the previous task (Figure 4.1-4.6).

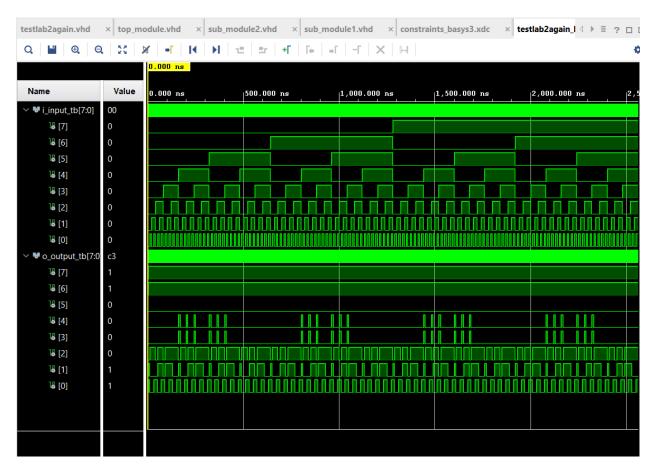


Figure 4.1: Simulation of the board state in Figure 3.1

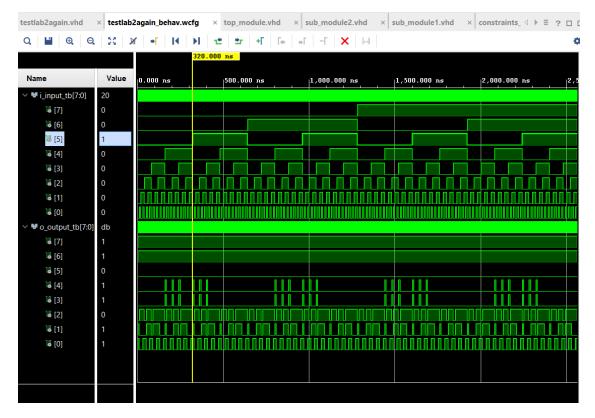


Figure 4.2: Simulation of the board state in Figure 3.2

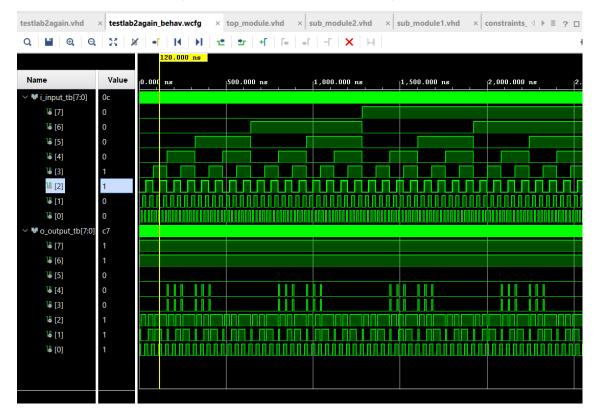


Figure 4.3: Simulation of the board state in Figure 3.3

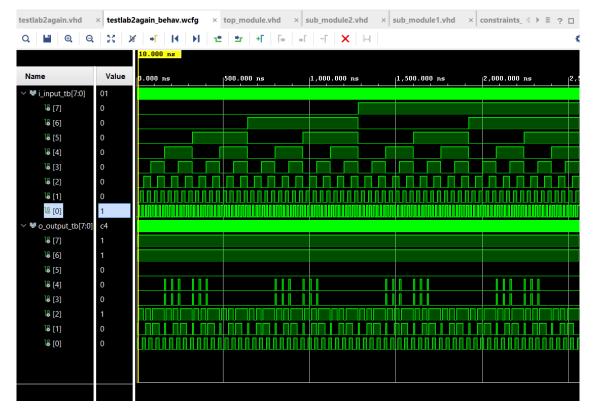


Figure 4.4: Simulation of the board state in Figure 3.4

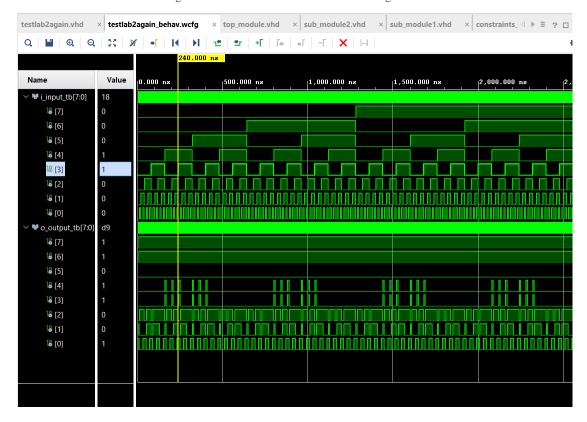


Figure 4.5: Simulation of the board state in Figure 3.5

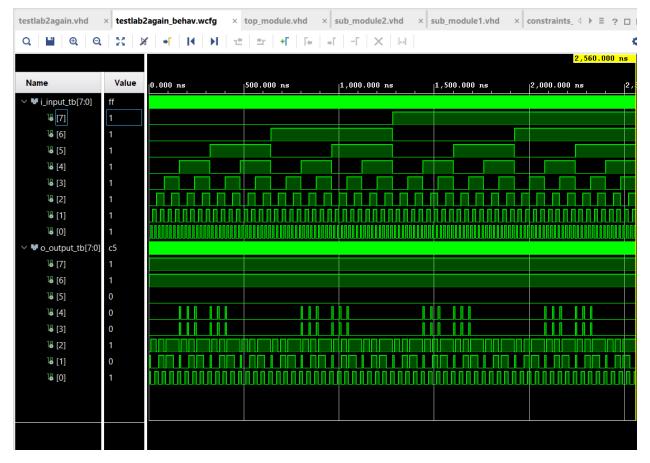


Figure 4.6: Simulation of the board state in Figure 3.6

Through analyzing each waveform, it was observed that for each input in the simulation matched the real-world LED output of the board. This meant that the simulation was successful and was working as expected.

Task-5) When each schematic was being generated, the program encountered zero errors. The RTL schematic (Figure 5.1) represents the three 2-input logic gates that were entered to the submodule inside the top module. This represents the main function of the program of getting inputs and processing them. The other schematics, the implemented and the synthesized schematic, represented the design tools structural layout as a logical function of eight binary input values (Figure 5.2). These schematics had the same representation since the project had no given time constraints and was made out of simple logic gates, making them identical in function.

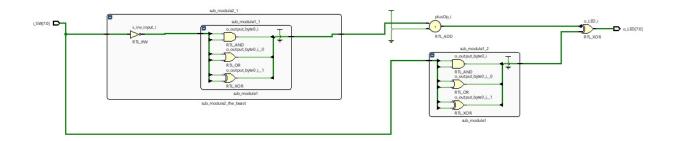


Figure 5.1: RTL Schematic

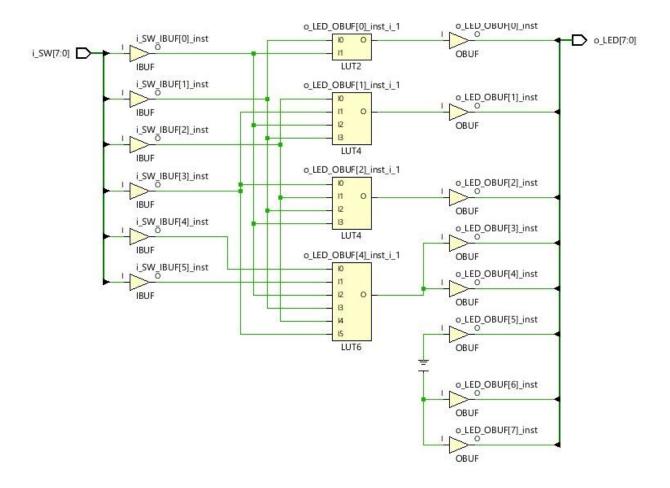


Figure 5.2: Implemented Schematic and Synthesized Schematic

Task-6) The following is every line of code that was used in the project:

#### top module.vhd

```
library IEEE;
use IEEE.STD LOGIC 1164.ALL;
use IEEE.NUMERIC STD.ALL;
entity top module is
  Port (
    i_SW: in STD_LOGIC_VECTOR (7 downto 0);
    o LED: out STD LOGIC VECTOR (7 downto 0)
  );
end top module;
architecture Structural top of top module is
  component sub module 1 is
    port (
      i input byte: in STD LOGIC VECTOR (7 downto 0);
      o output byte: out STD LOGIC VECTOR (7 downto 0)
    );
  end component sub module1;
  component sub module2 the beast is
    port (
      i switch inputs: in STD_LOGIC_VECTOR (7 downto 0);
      o output vector: out STD LOGIC VECTOR (7 downto 0)
    );
  end component sub module2 the beast;
  signal s output 1, s output 2: STD LOGIC VECTOR(7 downto 0) := (others => '0');
  signal s output 3
                        : unsigned(7 downto 0)
                                                 := (others => '0');
```

```
sub module1 2: sub module1
    port map (
      i input byte => i SW,
      o_output_byte => s_output_1
    );
  sub module2 1 : sub module2 the beast
    port map (
    i switch inputs => i SW,
    o output vector => s output 2
    );
  s output 3 <= unsigned(s output 2) + 25;
  o_LED <= (not std_logic_vector(s_output_3)) xor s_output_1;
end Structural top;
sub module1.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity sub module1 is
                           Port (
                             i_input_byte : in STD_LOGIC_VECTOR (7 downto 0);
                             o_output_byte : out STD_LOGIC_VECTOR (7 downto 0)
                           );
end sub_module1;
```

```
architecture Structural sub1 of sub module1 is
begin
                           o output byte(0)
                                                 <= i input byte(0) and i input byte(1); --Changed
three operators according to the table in the lab document
                           o output byte(1) <= i input byte(2) or i input byte(3);
                                                 <= i input byte(4) xor i input byte(5);
                           o output byte(2)
                           o output byte(5 downto 3) <= "010";
                           o output byte(7 downto 6) <= (others => '0');
end Structural sub1;
sub_module2_the_beast.vhd
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity sub module2 the beast is
  Port (
    i switch inputs: in STD LOGIC VECTOR (7 downto 0);
    o output vector: out STD LOGIC VECTOR (7 downto 0)
  );
end sub module2 the beast;
architecture Structural sub2 of sub module2 the beast is
  component sub module1 is
    port (
      i input byte : in STD_LOGIC_VECTOR (7 downto 0);
      o output byte: out STD LOGIC VECTOR (7 downto 0)
```

);

```
end component sub module1;
  signal s inv input: STD LOGIC VECTOR(7 downto 0) := (others => '0');
begin
  s inv input <= not i switch inputs;
  sub module1 1: sub module1
    port map (
      i_input_byte => s_inv_input,
      o_output_byte => o_output_vector
    );
end Structural sub2;
constraints_basys3.xdc
set_property PACKAGE_PIN V17 [get_ports {i_SW[0]}]
       set_property IOSTANDARD LVCMOS33 [get_ports {i_SW[0]}]
set_property PACKAGE_PIN V16 [get_ports {i_SW[1]}]
       set property IOSTANDARD LVCMOS33 [get ports {i SW[1]}]
set property PACKAGE PIN W16 [get ports {i SW[2]}]
       set property IOSTANDARD LVCMOS33 [get ports {i SW[2]}]
set property PACKAGE_PIN W17 [get_ports {i_SW[3]}]
       set property IOSTANDARD LVCMOS33 [get ports {i SW[3]}]
set_property PACKAGE_PIN W15 [get_ports {i_SW[4]}]
       set property IOSTANDARD LVCMOS33 [get_ports {i_SW[4]}]
set_property PACKAGE_PIN V15 [get_ports {i_SW[5]}]
       set property IOSTANDARD LVCMOS33 [get ports {i SW[5]}]
set_property PACKAGE_PIN W14 [get_ports {i_SW[6]}]
       set property IOSTANDARD LVCMOS33 [get ports {i SW[6]}]
set_property PACKAGE_PIN W13 [get_ports {i_SW[7]}]
       set property IOSTANDARD LVCMOS33 [get_ports {i_SW[7]}]
```

```
set property PACKAGE PIN U16 [get ports {o LED[0]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[0]}]
set property PACKAGE PIN E19 [get ports {o LED[1]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[1]}]
set property PACKAGE_PIN U19 [get_ports {o_LED[2]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[2]}]
set_property PACKAGE_PIN V19 [get_ports {o_LED[3]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[3]}]
set property PACKAGE PIN W18 [get ports {o LED[4]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[4]}]
set property PACKAGE PIN U15 [get ports {o LED[5]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[5]}]
set property PACKAGE PIN U14 [get ports {o LED[6]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[6]}]
set property PACKAGE PIN V14 [get ports {o LED[7]}]
      set property IOSTANDARD LVCMOS33 [get ports {o LED[7]}]
```

#### testlab2again.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.numeric_std.ALL;
-- default libraries are sufficient for this specific test bench
entity testlab2again is
end testlab2again;
```

Architecture Behavioral of testlab2again is

```
Component top module
Port(
i SW: in STD LOGIC VECTOR (7 downto 0);
o LED: out STD LOGIC VECTOR (7 downto 0)
);
end Component;
Signal i input tb: std logic vector (7 downto 0) := (others => '0');
-- initial inputs are taken as zero
Signal o output tb: std logic vector (7 downto 0):= (others => '0');
-- same as input testbench values since the same type and amount of data is expected
begin
UUT: top_module
--defining the module for the output
Port Map(
i SW => i input tb,
o LED => o output tb
--mapping each input and output to our design
);
stim proc: process
--actual process code for the testbench
begin
for s in 0 to 255 loop
--our range is defined for 8 binary vallues
 i input tb <= std logic vector(to unsigned(s,8));
```

```
--testbench input is assigned
wait for 10 ns;
--duration of each impusle is defined
end loop;
wait;
end process;
--program is finished
end Behavioral;
```

#### **Conclusion:**

The purpose of this laboratory assignment was to introduce basic concepts of FGPAs, VHDL and the BASYS3 board through debugging the main code and forming a testbench for simulations. After the main program was debugged out of six errors and simulated, an output determining real-world states of the logic board was formed. Additionally, through pre-experimentation research, certain programmable logic concepts were learnt such as port maps, testbenches and modules. The experiment also pushed experimenters to write individual testbench programs for general applications and signal generation applications.

### **References:**

Brown, S., & Vranesic, Z. (2023). Fundamentals of digital logic with VHDL design (4th ed.). McGraw-Hill.

Digilent, Inc. (n.d.). *Basys 3 reference manual*. Digilent. Retrieved February 19, 2025, from <a href="https://digilent.com/reference/programmable-logic/basys-3/reference-manual?srsltid=AfmBOorb8gUx">https://digilent.com/reference/programmable-logic/basys-3/reference-manual?srsltid=AfmBOorb8gUx</a> cAXfwmU4GnXTQ33cTBA0kqw2g9RZtoN0aPWdStd3ih6

Xilinx, Inc. (2022). Vivado synthesis: User guide (UG901). Xilinx. Retrieved February 19, 2025, from <a href="https://www.xilinx.com/support/documents/swmanuals/xilinx2022">https://www.xilinx.com/support/documents/swmanuals/xilinx2022</a> 2/ug901-vivado-synthesis.pdf